

Laboratory VIII

Discrete – Circuit MOSFET Amplifier

Build in Multisim the biasing scheme given in Fig. 2.

1. Determine the bias/quiescent point of the circuit by measuring the DC parameters V_{GS} , V_{DS} and I_D .
2. Determine the region in which the transistor is operating.
3. Determine the voltages at all nodes and the currents through all branches.

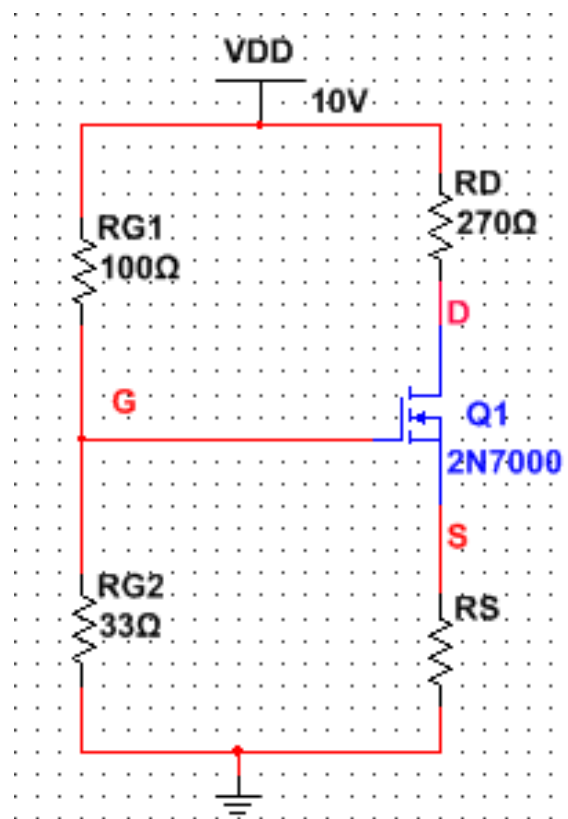


Figure 2: Biasing scheme

Discrete – Circuit MOSFET Amplifier

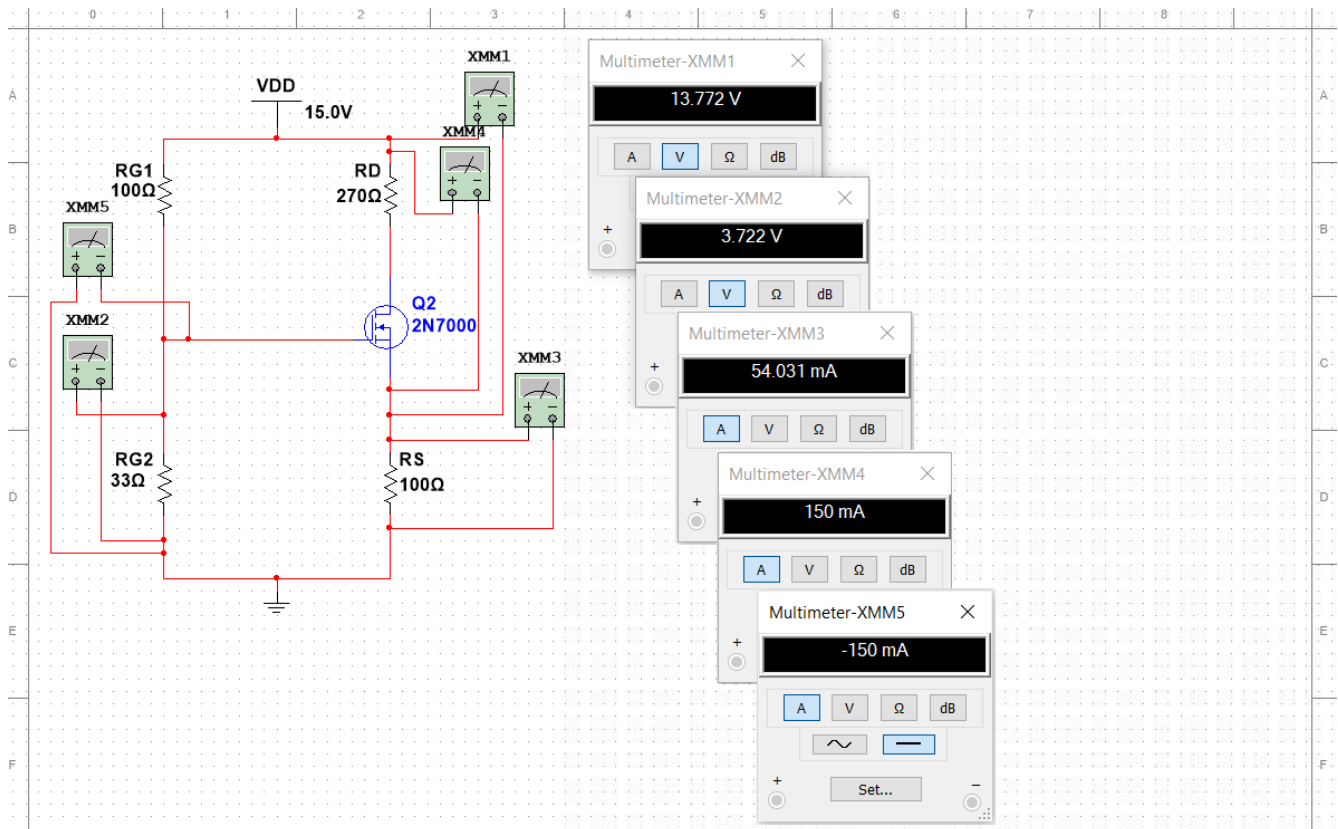


Fig. 1: Biasing Scheme


- a) Prompts: $V_G = 3.722\text{V}$, $V_D = 13.772\text{V}$, $V_S = 0.54031\text{V}$,
 $I_D = I_S = 0.15\text{A} \Rightarrow$ The source and drain currents are equal but opposite.

$$V_{GS} = V_G - V_S = 3.722\text{V} - 0.54031\text{V} = 3.18169\text{V}$$

$$V_{DS} = V_D - V_S = 13.772\text{V} - 0.54031\text{V} = 13.23169\text{V}$$

- b) $V_D = 13.772$, $V_G - V_{th} \Rightarrow 13.772 > 3.722 - V_{th}$:
 Saturation Region (Emitter Junction = Forward Biased,
 Collector Junction = Forward Biased, \Rightarrow Saturation Region)
- c) Voltages and currents are determined at Fig. 1

Simulation Link: [click here](#)

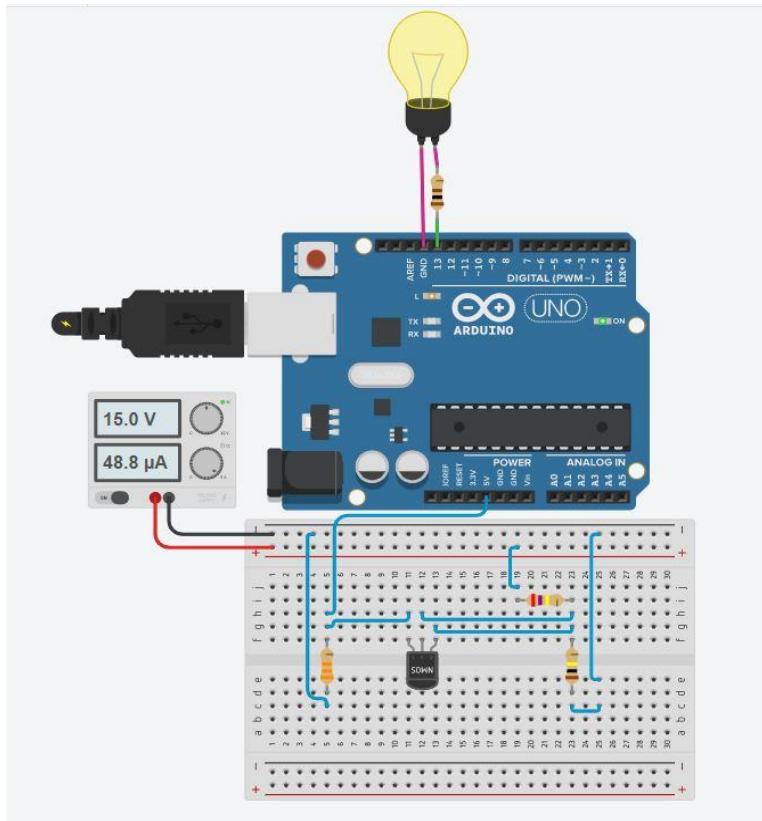

Arduino Code:

// C++ code

/*

This program blinks pin 13 of the Arduino (the built-in LED)

*/

void setup(){

pinMode(LED_BUILTIN, OUTPUT);

}

void loop(){

// turn the LED on (HIGH is the voltage level)

digitalWrite(LED_BUILTIN, HIGH);

delay(1000); // Wait for 1000 millisecond(s)

// turn the LED off by making the voltage LOW

digitalWrite(LED_BUILTIN, LOW);

delay(1000); // Wait for 1000 millisecond(s)

}